22 Lecture - PHY301

Important Mcqs

Which of the following is true about source transformation?

- A. It is used to replace a resistance with an equivalent source.
- B. It is used to replace a voltage source with an equivalent current source.
- C. It is used to replace a current source with an equivalent voltage source.
- D. It is used to replace a capacitor with an equivalent inductor.

Answer: B

What is the equivalent current source for a voltage source of 20V and resistance of 5??

- A. 5A
- B. 2A
- C. 4A
- D. 10A
- Answer: B

What is the equivalent voltage source for a current source of 3A and resistance of 2??

- A. 6V
- B. 1.5V
- C. 5V
- D. 7V

Answer: A

When should source transformation be used in circuit analysis?

- A. When there are only voltage sources in the circuit.
- B. When there are only current sources in the circuit.

- C. When there are both voltage and current sources in the circuit.
- D. When there are capacitors and inductors in the circuit.

Answer: C

What is the equation for calculating the current through a voltage source?

- A. I = V/R
- B. V = I * R
- C. R = V/I
- D. I = R/V
- Answer: A

What is the equation for calculating the voltage drop across a resistance?

- A. I = V/R
- B. V = I * R
- C. R = V/I
- D. I = R/V

Answer: B

What is the equivalent current source for a voltage source of 12V and resistance of 6??

- A. 2A
- B. 1.5A
- C. 4A
- D. 3A
- Answer: A

What is the equivalent voltage source for a current source of 5A and resistance of 3??

A. 15V

B. 8V

C. 3V

D. 1.5V

Answer: A

Which of the following is not an advantage of using source transformation in circuit analysis?

A. It simplifies the circuit.

- B. It reduces the number of different types of sources in the circuit.
- C. It makes analysis easier.
- D. It increases the complexity of the circuit.

Answer: D

What is the purpose of source transformation?

- A. To replace a resistance with an equivalent source.
- B. To replace a voltage source with an equivalent current source.
- C. To replace a current source with an equivalent voltage source.
- D. To replace an inductor with an equivalent capacitor.

Answer: B