

23 Lecture - PHY301

Important Mcqs

What is Thevenin's theorem?

- a. A theorem that simplifies complex circuits to a single voltage source and series resistance.
- b. A theorem that simplifies complex circuits to a single current source and parallel resistance.
- c. A theorem that calculates the current flowing in a circuit.

Solution: a

Who developed Thevenin's theorem?

- a. James Clerk Maxwell
- b. Charles Wheatstone
- c. Leon Charles Thevenin

Solution: c

What is the Thevenin resistance?

- a. The equivalent resistance of a circuit when all voltage sources are turned off and all current sources are shorted.
- b. The voltage between two points in a circuit when no current is flowing through the circuit.
- c. The equivalent resistance of a circuit when all voltage sources are turned on and all current sources are open.

Solution: a

How can we determine the Thevenin voltage of a circuit?

- a. By selecting two points in the circuit and assuming that all components to the right of these points are removed, leaving only the components to the left.
- b. By selecting two points in the circuit and assuming that all components to the left of these points are removed, leaving only the components to the right.
- c. By measuring the voltage at a single point in the circuit.

Solution: a

How can we determine the Thevenin resistance of a circuit?

- a. By selecting two points in the circuit and assuming that all components to the right of these points are removed, leaving only the components to the left.
- b. By selecting two points in the circuit and assuming that all components to the left of these points are removed, leaving only the components to the right.
- c. By measuring the resistance of a single component in the circuit.

Solution: a

Can Thevenin's theorem be used for AC circuits?

- a. Yes
- b. No

Solution: a

Can Thevenin's theorem be used for DC circuits?

- a. Yes
- b. No

Solution: a

What is the equivalent resistance of a circuit with only resistors in series?

- a. The sum of all the resistances.
- b. The reciprocal of the sum of the reciprocals of all the resistances.
- c. The difference between the highest and lowest resistance.

Solution: a

What is the equivalent resistance of a circuit with only resistors in parallel?

- a. The sum of all the resistances.
- b. The reciprocal of the sum of the reciprocals of all the resistances.
- c. The difference between the highest and lowest resistance.

Solution: b

What is the advantage of using Thevenin's theorem?

- a. It allows us to simplify complex circuits into simpler circuits, making it easier to analyze and understand them.
- b. It allows us to increase the voltage in a circuit.
- c. It allows us to decrease the resistance in a circuit.

Solution: a