6 Lecture - CS302

Important Subjective

1. What is a logic gate?

Answer: A logic gate is an electronic device that performs a logical operation on one or more input signals to produce an output signal.

2. What is a truth table?

Answer: A truth table is a table that lists all possible combinations of input values and their corresponding output values for a logic gate or circuit.

3. What is the difference between a combinational logic circuit and a sequential logic circuit?

Answer: A combinational logic circuit produces an output based solely on the current input values, while a sequential logic circuit produces an output based on both the current input values and the current state of the circuit.

4. What is the purpose of an inverter gate?

Answer: An inverter gate is used to invert or complement the input signal, producing an output that is the logical opposite of the input.

5. What is the difference between an AND gate and an OR gate?

Answer: An AND gate produces a high output only if all of its inputs are high, while an OR gate produces a high output if any of its inputs are high.

6. What is the propagation delay of a logic gate?

Answer: The propagation delay is the time it takes for a logic gate's output to respond to a change in its input.

7. What is the difference between positive logic and negative logic?

Answer: In positive logic, a high voltage represents a logical "1" and a low voltage represents a logical "0", while in negative logic, the opposite is true.

8. What is the function of a XOR gate?

Answer: A XOR gate produces a high output if the number of high inputs is odd, and a low output if the number of high inputs is even.

9. What is a decoder circuit?

Answer: A decoder circuit takes a binary input and produces one of several possible outputs based on the input value.

10. What is a multiplexer circuit?

Answer: A multiplexer circuit takes multiple input signals and selects one of them to pass through to the output based on a control signal.