7 Lecture - CS302

Important Mcqs

- 1. Which of the following is not a digital circuit component?
 - a) Resistor
 - b) Capacitor
 - c) Transistor
 - d) Logic gate

Answer: a) Resistor

- 2. What is the primary advantage of digital circuits over analog circuits?
 - a) Higher accuracy
 - b) Lower power consumption
 - c) Faster processing
 - d) All of the above

Answer: d) All of the above

- 3. Which of the following is not a basic logic gate?
 - a) XOR gate
 - b) NAND gate
 - c) INHIBIT gate
 - d) NOT gate

Answer: c) INHIBIT gate

- 4. What is the purpose of a decoder circuit?
 - a) To convert a binary input into one of several possible outputs
 - b) To combine multiple inputs into a single output
 - c) To provide a logical complement of the input signal
 - d) To amplify the input signal

Answer: a) To convert a binary input into one of several possible outputs

- 5. What is the propagation delay of a logic gate?
 - a) The amount of time it takes for a signal to travel through the gate
 - b) The amount of time it takes for the gate output to respond to a change in its input
 - c) The amount of time it takes for a gate to power up
 - d) The amount of time it takes for a gate to power down

Answer: b) The amount of time it takes for the gate output to respond to a change in its input

- 6. Which of the following is not an operational characteristic of digital circuits?
 - a) Output voltage
 - b) Timing characteristics
 - c) Frequency response
 - d) Power consumption

Answer: c) Frequency response

- 7. What is the purpose of a multiplexer circuit?
 - a) To convert a binary input into one of several possible outputs

- b) To combine multiple inputs into a single output
- c) To provide a logical complement of the input signal
- d) To select one of several input signals to pass through to the output

Answer: d) To select one of several input signals to pass through to the output

8. Which type of logic uses a high voltage to represent a logical "1"?

- a) Positive logic
- b) Negative logic
- c) Complementary logic
- d) None of the above

Answer: a) Positive logic

9. What is the primary purpose of simulation in digital circuit design?

- a) To test the circuit for reliability
- b) To optimize the circuit for power consumption
- c) To analyze the circuit's performance under different input conditions
- d) To manufacture the circuit components

Answer: c) To analyze the circuit's performance under different input conditions

10. Which of the following is not a common application of digital circuits?

- a) Computer systems
- b) Telecommunications
- c) Power generation
- d) Consumer electronics

Answer: c) Power generation