9 Lecture - CS302

Important Mcqs

- 1. What is the complement of the Boolean expression A + B?
 - A. A + B
 - B. AB
 - C. A' + B'
 - D. AB'

Solution: C

- 2. What is the output of the AND gate when both inputs are 1?
 - A. 0
 - B. 1
 - C. Undefined
 - D. Can't be determined

Solution: B

- 3. Which of the following laws of Boolean algebra is used to simplify the expression A(B+C)?
 - A. Associative law
 - B. Commutative law
 - C. Distributive law
 - D. DeMorgan's law

Solution: C

- 4. What is the output of the XOR gate when both inputs are 1?
 - A. 0
 - B. 1
 - C. Undefined
 - D. Can't be determined

Solution: A

- 5. What is the complement of the Boolean expression AB + C?
 - A. AB' + C' B. A' + B' + C' C. A + B' + C
 - D. AB' + C

Solution: B

Which of the following is a simplification technique used for Boolean expressions?
A. Truth table

B. Logic gate

C. Karnaugh map

D. Flip-flop

Solution: C

7. What is the output of the OR gate when both inputs are 0?

- A. 0
- B. 1
- C. Undefined
- D. Can't be determined

Solution: A

8. Which of the following is NOT a logical operator in Boolean algebra?

- A. AND
- B. OR
- C. XOR
- D. NOT

Solution: C

9. Which of the following is a property of DeMorgan's law?

A. A + 0 = A B. A + A' = 0 C. A(B+C) = AB + AC D. (A+B)' = A' . B'

Solution: B

10. What is the output of the NAND gate when both inputs are 0?

- A. 0
- B. 1
- C. Undefined
- D. Can't be determined

Solution: B