# **15 Lecture - CS302**

# **Important Mcqs**

- 1. What is the purpose of a BCD adder circuit?
  - A) To add two binary numbers
  - B) To add two decimal numbers
  - C) To add two BCD numbers
  - D) To subtract two BCD numbers

# Answer: C

### 2. Which type of logic gates are used in BCD adder circuit?

- A) AND gates
- B) OR gates
- C) XOR gates
- D) All of the above

### Answer: D

### 3. How many bits are required to represent a single BCD digit?

- A) 2
- B) 3
- C) 4
- D) 5

# Answer: C

#### 4. How many full adders are required to design a 4-bit BCD adder?

- A) 1
- B) 2
- Ć) 3
- D) 4

# Answer: 2

# 5. Which input(s) of a BCD adder are applied to the carry-in of the first full adder?

- A) The least significant bit (LSB) of both inputs
- B) The most significant bit (MSB) of both inputs
- C) The carry-out of the previous stage and the LSB of the current stage input
- D) None of the above

# Answer: D

# 6. What is the maximum sum that can be generated by a single BCD adder?

- A) 9
- B) 10

C) 15

D) 16

#### Answer: 9

7. What is the carry-out of a full adder when both inputs are 1?

A) 0

B) 1

Ć) 2

D) Cannot be determined

#### Answer: 1

- 8. Which type of multiplexer is used in BCD adder to select between the carry-in and sum output of the full adder?
  - A) 2:1
  - B) 4:1
  - C) 8:1
  - D) 16:1

#### Answer: A

#### 9. What is the purpose of the parity generator in BCD adder circuit?

- A) To check for errors in the input data
- B) To ensure that the output is a valid BCD number
- C) To generate a parity bit for error detection
- D) None of the above

#### Answer: B

#### 10. What is the maximum number of BCD digits that can be added using an 8-bit BCD adder?

- A) 1
- B) 2
- C) 4
- D) 8

Answer: 2