18 Lecture - CS302

Important Subjective

1. What is a 2-input 4-bit multiplexer?

Answer: A 2-input 4-bit multiplexer is a digital logic circuit that has four data inputs and two selection inputs, and selects one of the four inputs based on the values of the selection inputs.

2. What is the purpose of a 2-input 4-bit multiplexer?

Answer: The purpose of a 2-input 4-bit multiplexer is to select one input from multiple inputs based on the values of the selection inputs, and to output the selected input.

3. How many data inputs does a 2-input 4-bit multiplexer have?

Answer: A 2-input 4-bit multiplexer has four data inputs.

4. How many selection inputs does a 2-input 4-bit multiplexer have?

Answer: A 2-input 4-bit multiplexer has two selection inputs.

5. What is the maximum number of inputs that a 2-input 4-bit multiplexer can select from?

Answer: A 2-input 4-bit multiplexer can select from a maximum of four inputs.

6. How is the output of a 2-input 4-bit multiplexer determined?

Answer: The output of a 2-input 4-bit multiplexer is determined by the values of the selection inputs, which select one of the four data inputs to be output.

- 7. What is the truth table for a 2-input 4-bit multiplexer? Answer: The truth table for a 2-input 4-bit multiplexer has four rows and eight columns.
- 8. What is the advantage of using a 2-input 4-bit multiplexer in digital circuits? Answer: The advantage of using a 2-input 4-bit multiplexer in digital circuits is that it reduces circuit complexity by selecting one input from multiple inputs.

9. What are the typical applications of a 2-input 4-bit multiplexer?

Answer: The typical applications of a 2-input 4-bit multiplexer include signal routing, data compression, and address decoding.

10. How is a 2-input 4-bit multiplexer different from a demultiplexer?

Answer: A 2-input 4-bit multiplexer selects one input from multiple inputs, while a demultiplexer selects one output from multiple outputs.