20 Lecture - CS302

Important Subjective

- 1. How can a pull-up resistor be used to implement a constant 1 signal? Answer: A pull-up resistor is connected between the signal line and the power supply voltage. This ensures that when the input signal is not connected, the voltage at the signal line is at a high level, which is interpreted as a constant 1 signal.
- 2. How can a pull-down resistor be used to implement a constant 0 signal? Answer: A pull-down resistor is connected between the signal line and the ground. This ensures that when the input signal is not connected, the voltage at the signal line is at a low level, which is interpreted as a constant 0 signal.
- 3. What is the function of a logic gate output connection to implement a constant signal? Answer: A logic gate output can be connected to either the power supply voltage or ground to implement a constant 1 or 0 signal, respectively.
- 4. Why is it important to implement constant signals in digital circuits? Answer: Constant signals are used as control signals and inputs to digital circuits. Implementing constant signals ensures that the signal does not fluctuate and remains at a constant level, which is important for the proper operation of the circuit.
- 5. What type of resistor is commonly used for pull-up or pull-down resistors? Answer: Carbon resistors are commonly used for pull-up or pull-down resistors.
- 6. What is the purpose of a pull-up or pull-down resistor? Answer: The purpose of a pull-up or pull-down resistor is to ensure a constant input signal, even when the input is not connected to a signal source.
- 7. In which type of circuit is the implementation of constant signals particularly important? Answer: The implementation of constant signals is particularly important in microprocessor circuits, where accurate and stable signals are crucial for proper operation.
- 8. How can a pull-up or pull-down resistor affect the signal level at the input of a circuit? Answer: A pull-up or pull-down resistor can affect the signal level at the input of a circuit by pulling the voltage level towards the power supply or ground, respectively.
- 9. What is the value of a pull-up resistor? Answer: A pull-up resistor has a high resistance value, typically in the range of several kilo-ohms to several mega-ohms.
- 10. What is the value of a pull-down resistor? Answer: A pull-down resistor has a low resistance value, typically in the range of several ohms to several kilo-ohms.