# 27 Lecture - CS302

## **Important Mcqs**

#### 1. What is a down counter?

- a) A digital circuit that counts up from a specified initial value to a maximum value
- b) A digital circuit that counts down from a specified initial value to zero
- c) A digital circuit that counts up or down depending on the input signal
- d) A digital circuit that counts at a constant rate

Answer: b) A digital circuit that counts down from a specified initial value to zero

## Which type of counter is commonly used in synchronous down counters?

- a) Flip-flops
- b) Schmitt triggers
- c) Shift registers
- d) Multiplexers

Answer: a) Flip-flops

### What is the maximum count that a 4-bit down counter can achieve?

- a) 7
- b) 8
- c) 15
- d) 16

Answer: b) 8

## What is the purpose of a presettable down counter?

- a) To count down from a specified initial value
- b) To count up to a specified final value
- c) To count up or down depending on the input signal
- d) To count at a constant rate

Answer: a) To count down from a specified initial value

#### Which type of down counter is also known as a binary ripple counter?

- a) Synchronous down counter
- b) Asynchronous down counter
- c) Presettable down counter
- d) Decade counter

Answer: b) Asynchronous down counter

#### Which input signal is used to enable a down counter?

- a) Clock
- b) Clear
- c) Load
- d) Count

Answer: a) Clock

Which type of down counter is commonly used in frequency dividers?

- a) Synchronous down counter
- b) Asynchronous down counter
- c) Presettable down counter
- d) Decade counter

## Answer: a) Synchronous down counter

### What is the output of a down counter when the count reaches zero?

- a) High
- b) Low
- c) Depends on the circuit design
- d) No output

## Answer: b) Low

## Which statement is true for a down counter with an active-high clock input?

- a) The count decreases on the rising edge of the clock
- b) The count decreases on the falling edge of the clock
- c) The count increases on the rising edge of the clock
- d) The count increases on the falling edge of the clock

Answer: b) The count decreases on the falling edge of the clock

## Which statement is true for a down counter with an active-low clear input?

- a) The counter is cleared on the rising edge of the clear input
- b) The counter is cleared on the falling edge of the clear input
- c) The counter is not affected by the clear input
- d) The counter is cleared when the clear input is high

Answer: d) The counter is cleared when the clear input is high