32 Lecture - CS302

Important Mcqs

1. What is the primary use of a D flip-flop in digital circuit design?

- a) To store a single bit of information
- b) To perform arithmetic operations
- c) To convert analog signals to digital signals
- d) To generate clock signals

Answer: a

How many inputs does a D flip-flop have?

- a) 1
- b) 2
- c) 3
- d) 4

Answer: b

What happens when the clock input of a D flip-flop transitions from low to high?

- a) The current state is transferred to the next state output
- b) The next state is transferred to the current state output
- c) The D input is ignored
- d) The Q output is inverted

Answer: a

Which of the following can be implemented using D flip-flops?

- a) Registers
- b) Counters
- c) Shift registers
- d) All of the above

Answer: d

How are the logic equations for the D inputs of flip-flops derived?

- a) By analyzing the clock signal
- b) By analyzing the present state
- c) By analyzing the input signal
- d) By using the Next-State Table

Answer: d

What is the purpose of the clock signal in a D flip-flop circuit?

- a) To generate output signals
- b) To synchronize state transitions
- c) To provide power to the circuit
- d) To provide feedback to the input

Answer: b

How many outputs does a D flip-flop have?

a) 1

- b) 2
- c) 3
- d) 4

Answer: b

Which of the following is true about D flip-flops?

- a) They are used to implement combinational logic
- b) They are used to implement memory elements
- c) They are used to convert analog signals to digital signals
- d) They are used to generate clock signals

Answer: b

What is the advantage of using D flip-flops in digital circuit design?

- a) They provide a simple and reliable way to store a single bit of information
- b) They are faster than other types of flip-flops
- c) They require fewer gates to implement
- d) They consume less power than other types of flip-flops

Answer: a

How can D flip-flops be cascaded together?

- a) By connecting their clock inputs together
- b) By connecting their data inputs together
- c) By connecting their output signals together
- d) By connecting their enable inputs together

Answer: c