

# 37 Lecture - CS302

## Important Subjective

1. **What is an input latch in a digital circuit, and how does it work?**

Answer: An input latch is a logic circuit that stores data temporarily. It consists of a flip-flop and a latch enable input. When the latch enable input is high, the input data is latched, and the output remains stable until the latch enable input is low again.

**Why is reducing the number of input latches in a digital circuit important?**

Answer: Reducing the number of input latches simplifies the circuit, reduces power consumption, and makes it easier to test and debug.

**What are some common techniques used to reduce the number of input latches in a digital circuit?**

Answer: Some common techniques include multiplexing, decoders, and state machines.

**What is the trade-off when reducing the number of input latches in a digital circuit?**

Answer: The trade-off is that the circuit becomes less flexible and has reduced functionality.

**How can reducing the number of input latches affect the performance of a digital circuit?**

Answer: Reducing the number of input latches can improve the performance of a digital circuit by reducing its complexity and power consumption.

**What are some applications where reducing the number of input latches is particularly important?**

Answer: Applications where power consumption is critical, such as mobile devices, wearables, and IoT devices.

**What are the advantages of using state machines to reduce the number of input latches in a digital circuit?**

Answer: State machines can reduce the number of input latches by using fewer inputs to encode a sequence of states.

**What is multiplexing, and how can it reduce the number of input latches in a digital circuit?**

Answer: Multiplexing is a technique that uses fewer input signals to select between multiple inputs. It can reduce the number of input latches by combining multiple inputs into a single signal.

**What are the disadvantages of reducing the number of input latches in a digital circuit?**

Answer: The main disadvantage is reduced flexibility and functionality.

**What are some considerations that designers must take into account when reducing the number of input latches in a digital circuit?**

Answer: Designers must consider the trade-offs between functionality, performance, power consumption, and cost. They must also ensure that the reduced number of input latches does

not compromise the circuit's ability to perform its intended function.